

ECE 124A

VLSI Principles


Lecture 10

Prof. Kaustav Banerjee
Electrical and Computer Engineering
E-mail: kaustav@ece.ucsb.edu

Designing Sequential Logic Circuits

Sequential Logic

 All useful systems require storage of state information....



A generic Finite State Machine (FSM) consisting of combinational logic and registers.

Output of the FSM = $F(\text{current inputs}, \text{current state})$

Next State is determined based on current state and current inputs—fed to the input (D) of the registers

Note: There are 2 storage mechanisms: 1) positive feedback and 2) charge storage

Classification of Memory Elements

- Background Memory: large centralized memory core (high density array structures)---SRAMs and DRAMs
- Foreground Memory: embedded in a logic (individual registers or register banks)—**focus of this section**

Classification of Memory Elements

Static Memory:

- ❑ preserves state as long as **power is ON**
- ❑ built by using **positive feedback or regeneration** where the circuit consists of intentional connections between the output and input of a combinational circuit
- ❑ most useful when register will **not be updated for extended periods of time** (eg., configuration data loaded at power-up time).
- ❑ Condition also holds for most processors that use **conditional clocking**, (gated CLK) where the CLK is turned off for unused modules----**no guarantee on how frequently the registers will be clocked and static memories are needed to state information.**
- ❑ **bistable element** is the most popular form

Classification of Memory Elements

Dynamic Memory:

- ❑ store data for short (ms) period of time
- ❑ based on the principle of **temporary charge storage** on parasitic capacitors in MOS devices
- ❑ similar to **dynamic** logic..... capacitors need to be refreshed periodically to compensate for charge leakage
- ❑ significantly simpler----hence, provide **higher performance** and **lower power dissipation**
- ❑ most useful in **datapath circuits** that require higher performance levels and are **periodically clocked**

Naming Conventions

□ Definitions:


- a latch is a **level sensitive device**
- a register is an **edge-triggered storage element**

□ There are many different naming conventions

- For instance, many books call edge-triggered elements **flip-flops**
- This may lead to confusion however...
- Any **bistable** component formed by the cross coupling of gates is a **flip-flop** (FF)

Latches

Multiplexer based

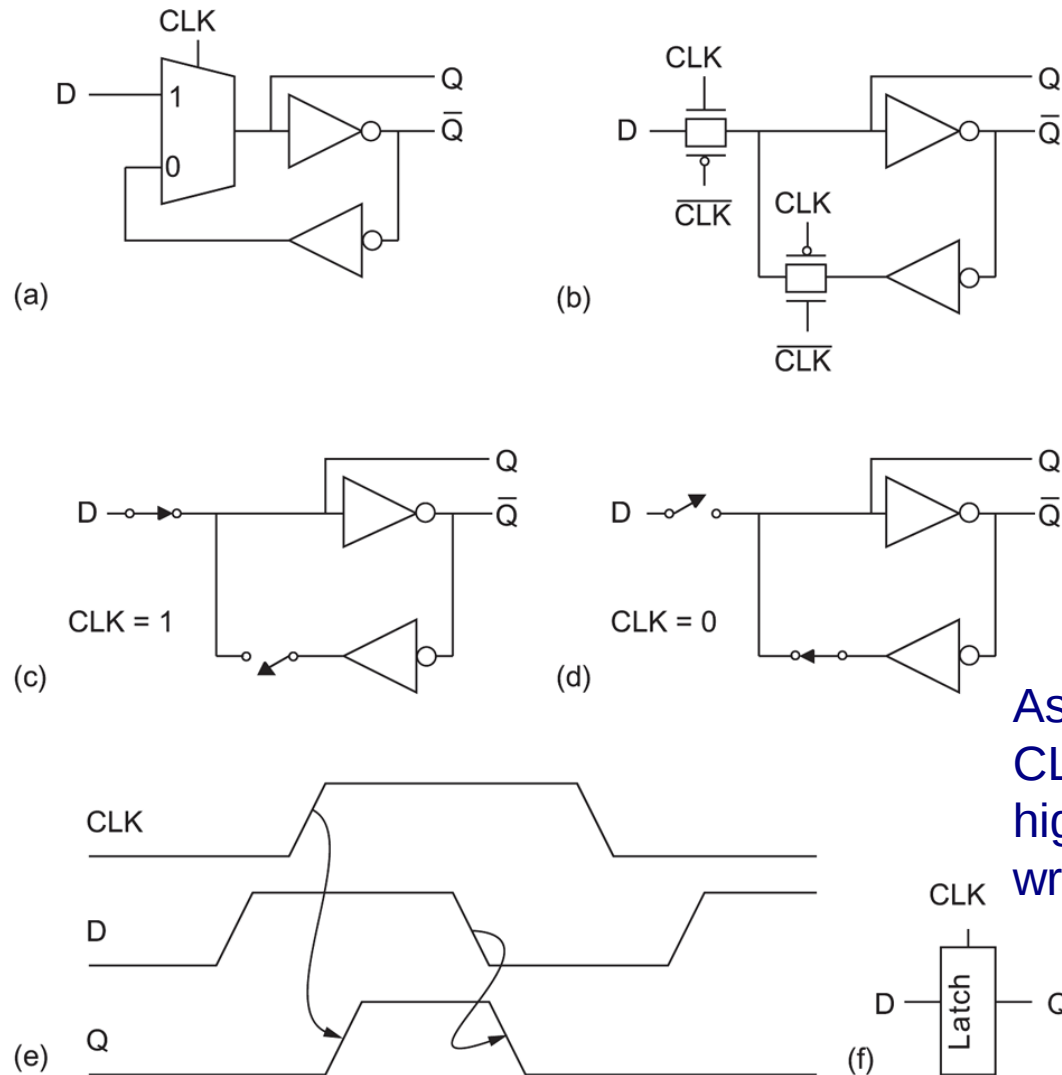

CLK=1: D to Q


CLK=0: Holds state of Q

As long as CLK remains high, D will be written on Q


FIG 1.30 CMOS positive-level-sensitive D latch

Timing of P/N Latches

Positive Latch

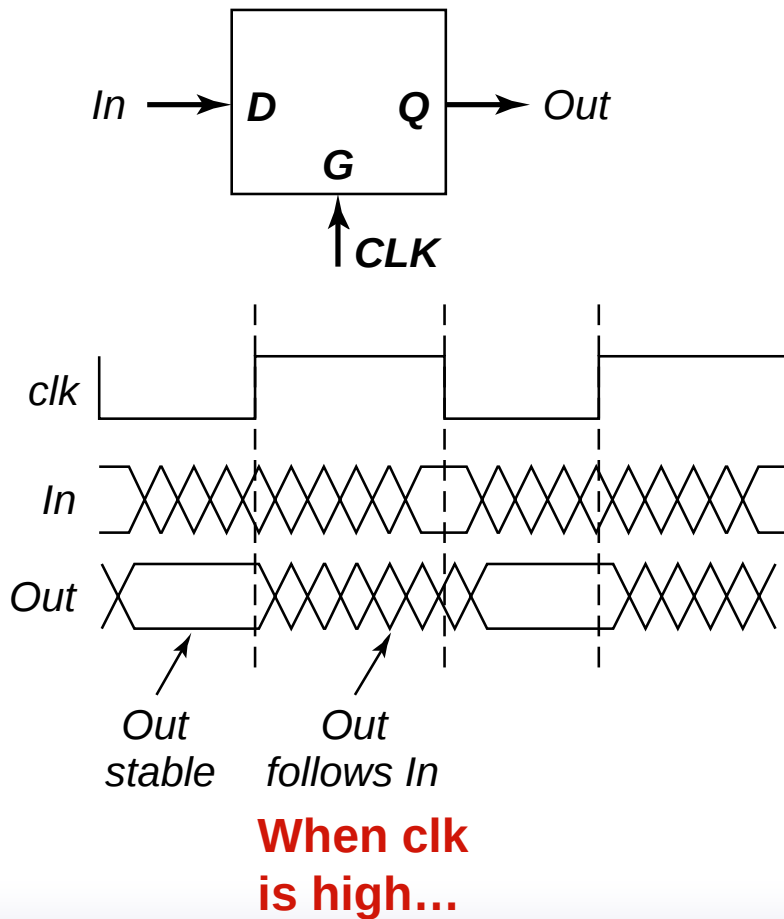


Negative Latch

 

Latch-Based Design

- N (negative) latch is transparent when $\phi = 0$


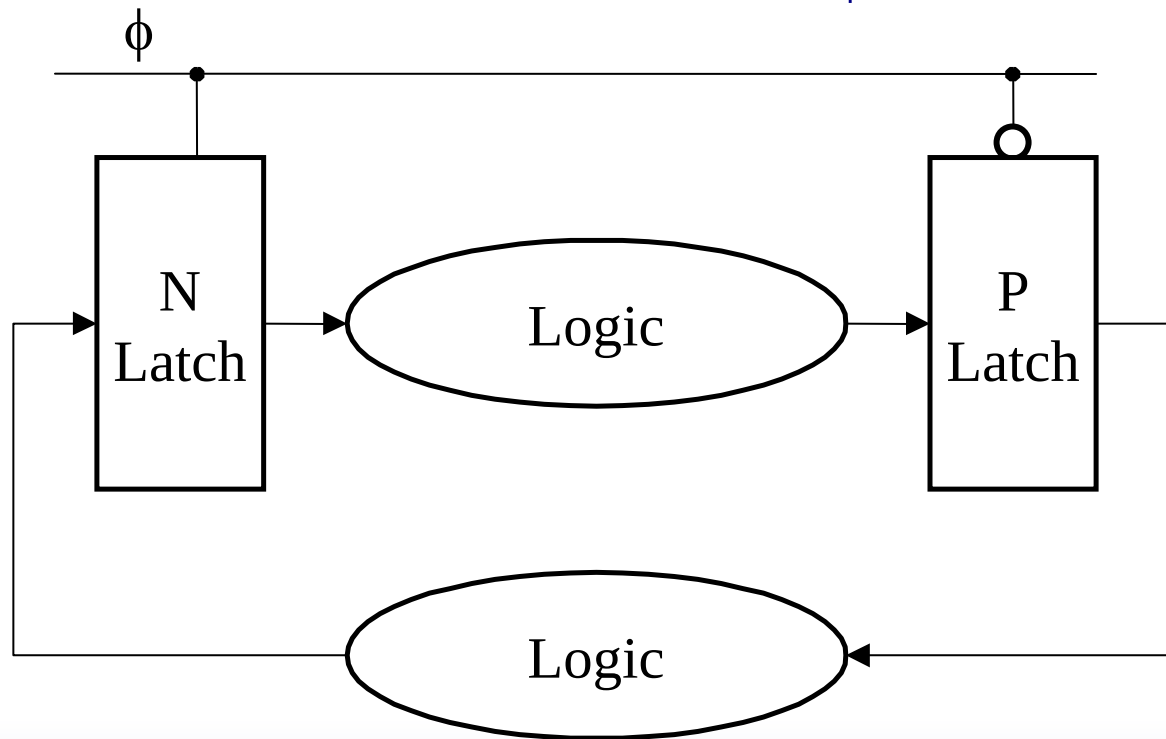
- P (positive) latch is transparent when $\phi = 1$



Latch versus Register



❑ Latch

stores data when
clock is low (or high)

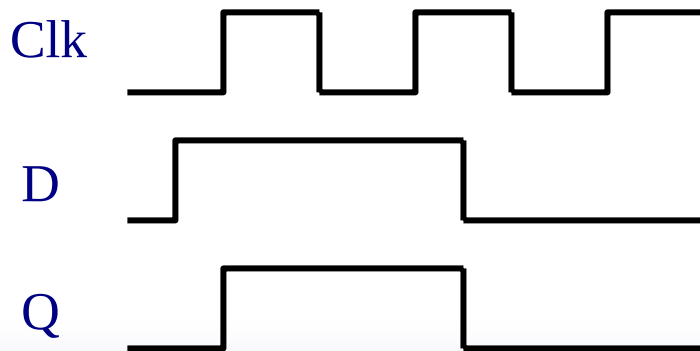 

❑ Register

stores data when
clock rises (or falls)

  

Registers or Flip-Flops

Combines two latches:

One +ve sensitive (slave) and one -ve sensitive latch (master)

Edge Triggered FF or Master-Slave FF

$CLK=0$: D to QM

$$\overline{QM} = \overline{D}$$

Slave holds previous value of Q

$CLK=1$: master can't sample input and holds value of D

Slave opens and $QM=(D) = Q$


 
 


FIG 1.31 CMOS positive-edge-triggered D flip-flop

Timing Definitions

 


t_{su} = **setup time** = time for which the data inputs (D) must be valid before the CLK edge

t_{hold} = **hold time** = time for which data input must remain valid after the CLK edge


t_{c2q} = **worst case** propagation time through the Register (w.r.t the CLK edge)

Characterizing Timing

Register


 


Latch

 

Requires an extra
timing parameter...

Maximum Clock Frequency

  

To ensure that the input data of the sequential elements is held long enough after the CLK edge and is not modified too soon by the new wave of data coming in:

$$2) t_{cdreg} + t_{cdlogic} > t_{hold}$$



t_{cd} : contamination delay
= minimum delay

$$1) T_{min} = t_{clk-Q} + t_{p,comb} + t_{setup}$$

Clk period must accommodate the longest delay of any stage in the network

Static Latches and Registers



Positive Feedback: Bi-Stability

  

A, B, and C are the three possible operating points

If gain > 1 in the transient region: A and B are the only stable operating points, C is a metastable point


Meta-Stability

  

- Gain is larger than 1 in the transition region
- Every small deviation causes the operation point to move away from its original bias point, C ---metastable

Flip-Flop

 
A cross coupled pair of inverters results in a bistable circuit...



- ❑ A FF is a bistable circuit, which has 2 stable states
- ❑ In the absence of triggering the circuit remains in a single state
- ❑ The state can be changed by applying an external trigger
- ❑ Two ways to achieve a change of state:
 - **Cut the feedback loop:** so that a new value can be written into **out** or **Q**
 - **This is MUX based: $Q = \text{CLK} \cdot Q + \text{CLK} \cdot \text{In}$ (most common)**
 - **Overpower the feedback loop**
 - Apply a trigger signal at the input of the FF and force the new value into the cell by overpowering the stored value
 - Needs careful sizing of transistors in the feedback loop and the trigger circuit
 - Used mostly in static background memories


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 

$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$



Positive latch
(transparent when CLK= 1)

 

$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Writing into a Static Latch

  Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states




Forcing the state

MUX based (not so efficient..# of
transistors driven by CLK is
high= 4)

→ (can implement as NMOS-only)

Mux-Based Latch

 


*CLK is driving several transistors with activity=1
(not good from power perspective!)*

Mux-Based Latch

NMOS only Pass Transistor

Reduces CLK load

 


When $CLK=1$, latch samples input D



$CLK=0$ enables feedback loop, puts latch in hold mode

Use of PT degrades NM and switching performance by passing $V_{dd}-V_{Tn}$ to the input of first inverter + static power (PMOS of inverter is never fully turned off)

Non-overlapping clocks

 

Master-Slave (Edge-Triggered) Register

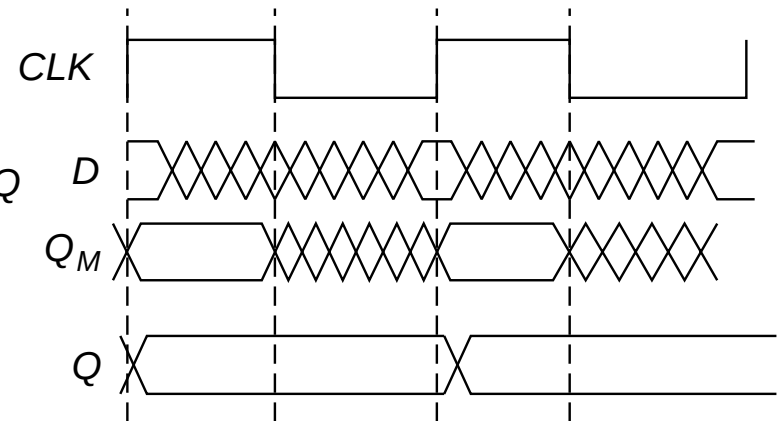 

CLK=0: master is transparent and D is copied to Q_M

During this time slave is in hold mode

As CLK=1: slave starts sampling, master in hold mode


Value of Q =Value of D right before the rising edge of the CLK: **+ve edge triggered effect**

Two opposite latches trigger on edge
Also called master-slave latch pair

Master-Slave +ve Edge Triggered Register

Transistor Level Implementation

X-gate Multiplexer-based latch pair

 

CLK=0: T_1 is on, T_2 is off, D input sampled onto Q_M


T_3 off and T_4 on: I_5 and I_6 hold the state of the Slave

CLK=1: T_3 is on, T_4 is off, Q_M sampled onto Q

T_2 on and T_1 off: I_2 and I_3 hold the state of Q_M

Master-Slave +ve Edge Triggered Register

Transistor Level Implementation

 

T_{c-q} = delay through T3 and I6 =

$$T_{c-q} = t_{pd_inv} + t_{pd_tx}$$

Since delay of I2 is included in set-up time output of I4 is valid before the rising edge of CLK

t_{su} = set-up time = time before the rising edge of the CLK during which the D input should remain stable so that Q_M samples the value reliably

Since D must propagate through I1, T1, I3, and I2 before the rising edge


$$t_{su} = 3t_{pd_inv} + t_{pd_tx}$$

$$t_{hold} = 0 \text{ (since T1 is cut off after CLK edge)}$$


↖ To ensure equal node voltages on both sides of the Xgate

Timing Analysis: Setup Time

 SPICE Simulations: progressively skew the input w.r.t CLK edge until the circuit fails



 (a) $T_{\text{setup}} = 0.21 \text{ nsec}$




(b) $T_{\text{setup}} = 0.20 \text{ nsec}$

CLK is enabled before the voltage across T₂ settles to the same value

Set-up time for this circuit = 210 ps and hold time = 0

Clk-Q Delay

 
t_{c-q} = 50% point of CLK to 50% point of Q



Reduced Clock Load Master-Slave Register


Ratioed circuit: provides reduced load at the cost of NM

 Note: X-gate register presents high capacitive load to the CLK signal



- Cons:** 1) I_1 must overpower I_2 to switch the state of the cross-coupled inverter
2) Reverse conduction-second stage can affect the state of the first latch (I_1 - I_2)
 I_4 must be a weak gate....


Avoiding Clock Overlap

 

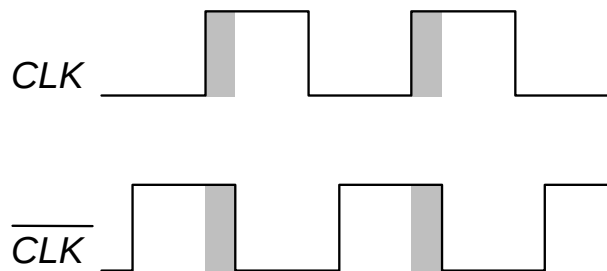(a) Schematic diagram of an NMOS only -ve M-S register

RACE Condition: If CLK and $\overline{\text{CLK}}$ are both ON for a short time, both sampling pass transistors are ON providing a direct path from D to Q. Hence, data at the output can change at the rising CLK edge

Also node A can be driven by both D and B: undefined state





(b) Overlapping clock pairs

Clock skew is a problem!

One Solution: use non-overlapping CLKs

Overpowering the Feedback Loop — Cross-Coupled Pairs

NOR-based set-reset

  

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State


Use external triggers, S and R to change state:

$S=1$ forces $Q=1$,

$R=1$ forces $Q=0$

Cross-Coupled NAND


Cross-coupled NANDs

 

This is not used in datapaths any more, but is a basic building memory cell


Transistor sizing is essential to ensure FF transition:

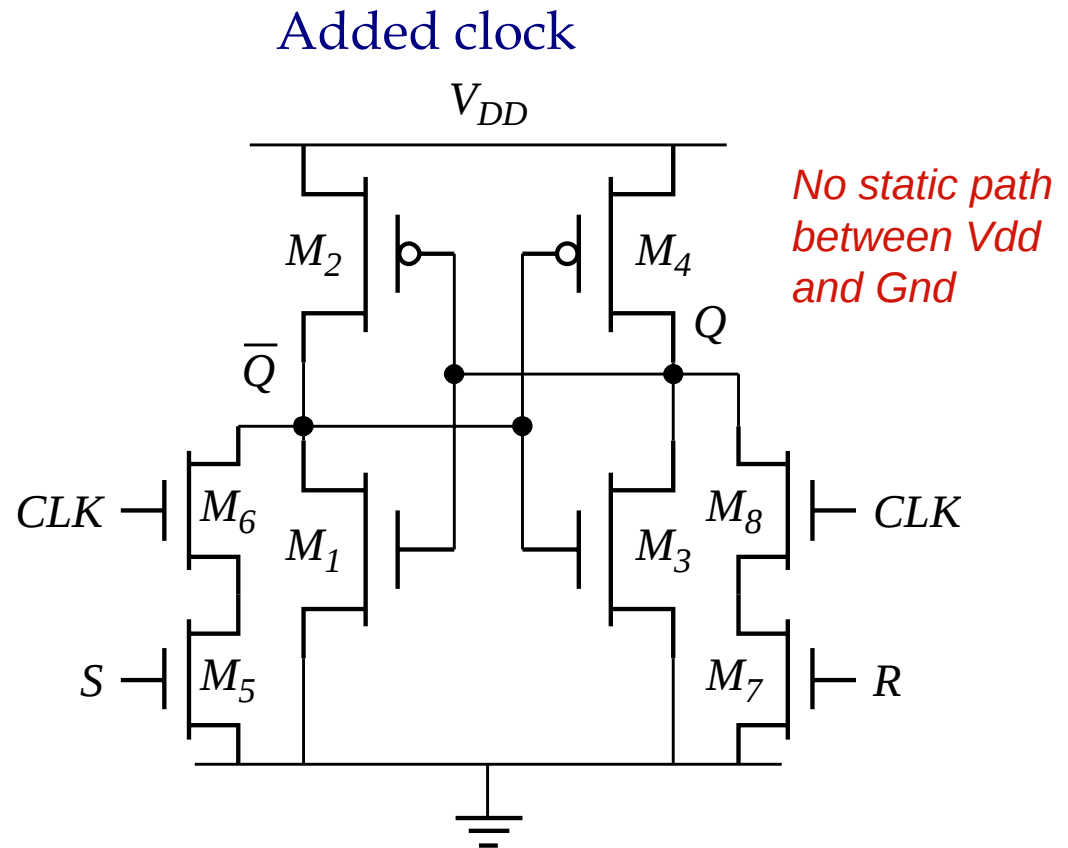If Q is high and R=1, then V_Q must be < V_M of INV M1-M2. Similar condition is needed to switch INV M3-M4 for S=1. This means we must increase the sizes of M5, M6, M7 and M8. M4-M7-M8 (and M5-M6-M2) form ratioed inverters.




Sizing Issues

0.25 μ m process

 

 Output voltage dependence
on transistor width



Transient response