


# *ECE 225*

# *High-Speed Digital IC Design*

## *Lecture 4*

Prof. Kaustav Banerjee  
Electrical and Computer Engineering  
*E-mail: [kaustav@ece.ucsb.edu](mailto:kaustav@ece.ucsb.edu)*

# MOS Transistor as a Switch

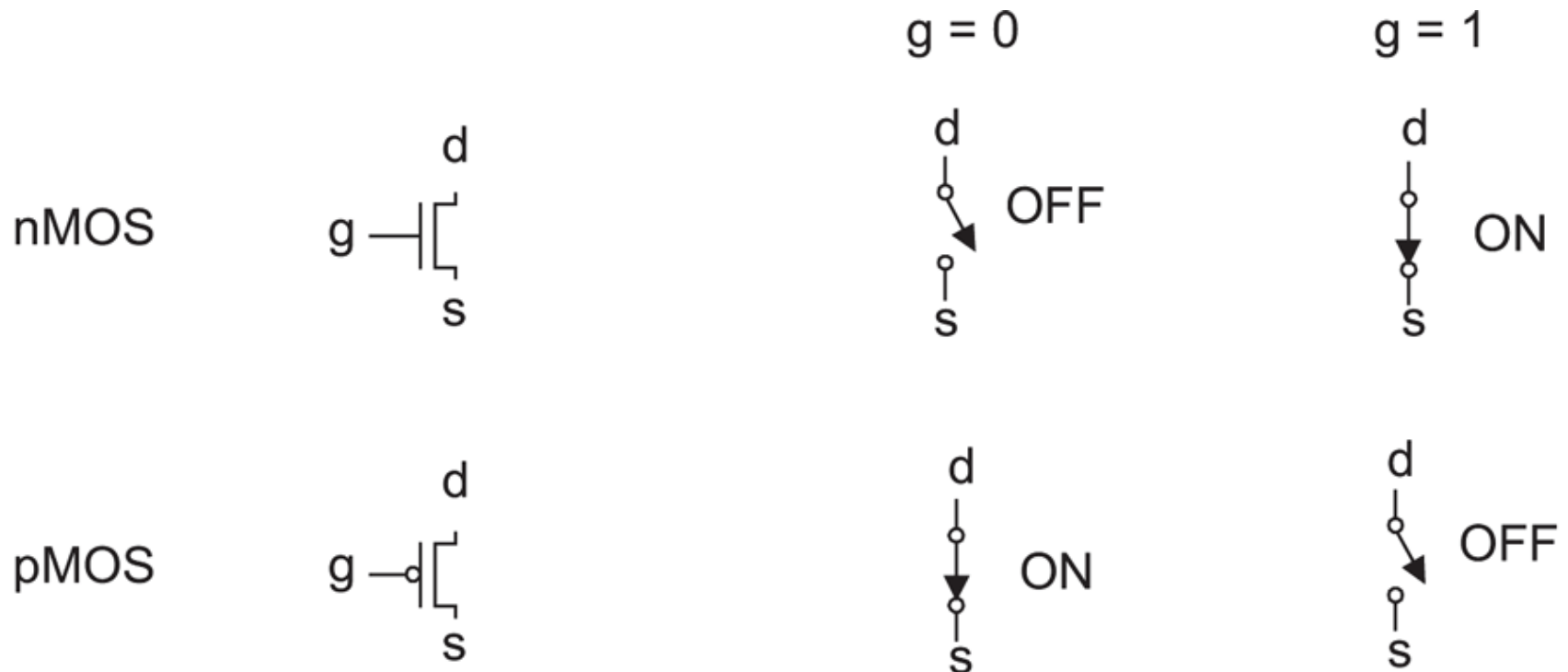


**FIG 1.9** Transistor symbols and switch-level models

# *Inverter (NOT Gate)*


| Table 1.1 Inverter truth table |   |
|--------------------------------|---|
| A                              | Y |
| 0                              | 1 |
| 1                              | 0 |

# Transistor Level Implementation

CMOS: Complementary MOS

 

(a)

 



(b)

**FIG 1.10** Inverter schematic (a) and symbol (b)  $Y = \overline{A}$
 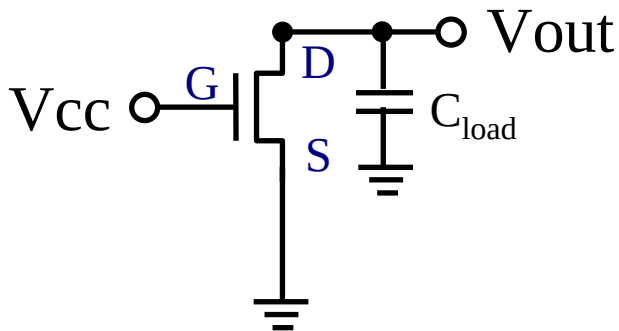
# MOS voltage levels

Case 1: NMOS discharges capacitor

- Initially:  $V_{out} = V_{cc}$  (capacitor fully charged)
- $V_{GS}$  of NMOS =  $V_{cc}$
- What is final  $V_{out}$ ?





- NMOS remains on since  $V_{GS} > V_T$
- Final output voltage  $V_{out} = 0V$
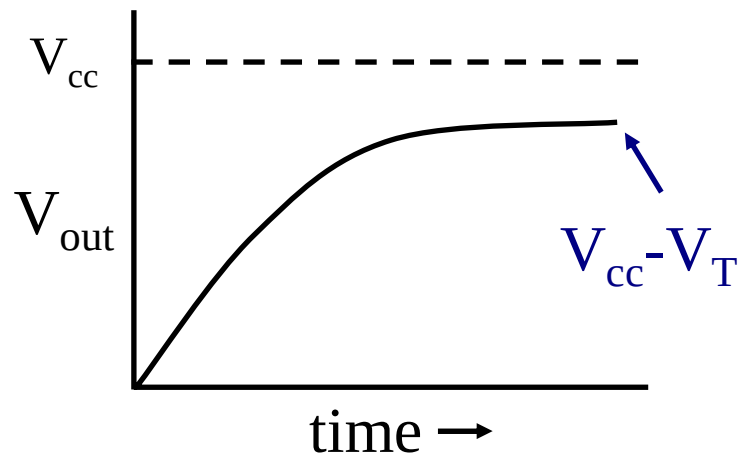 
# MOS voltage levels

Case 2: NMOS charges capacitor

- Initially:  $V_{out} = 0$
- Initial  $V_{GS}$  of NMOS =  $V_{cc}$
- What is final  $V_{out}$ ?




- NMOS remains on until  $V_{GS} = V_T$
- Final output voltage  $V_{out} = V_{cc} - V_T$

# MOS voltage levels


Repeat for PMOS:

□ Case 1: PMOS discharging capacitor

 

- PMOS on until  $V_{GS} = V_T$
- $V_{out} = |V_T|$

□ Case 2: PMOS charging capacitor

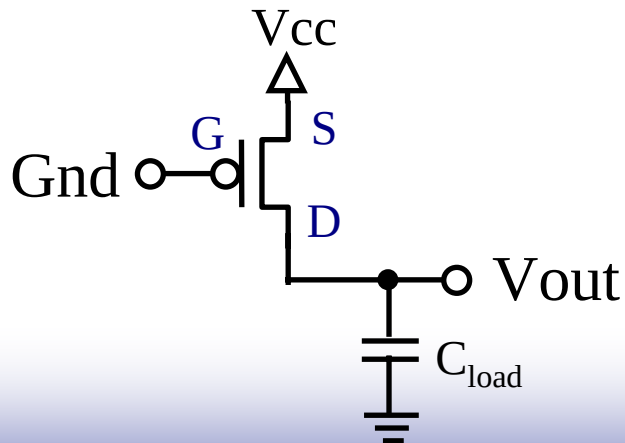

- PMOS always on ( $V_{GS} = -V_{CC}$ )
- $V_{out} = V_{CC}$

# *MOS voltage levels*

## □ NMOS summary

- Transfers logic '0' completely (good for discharging a node)
- Does not transfer logic '1' completely (bad for charging a node)


## □ PMOS summary

- Transfers logic '1' completely
- Does not transfer logic '0' completely

## □ Result:

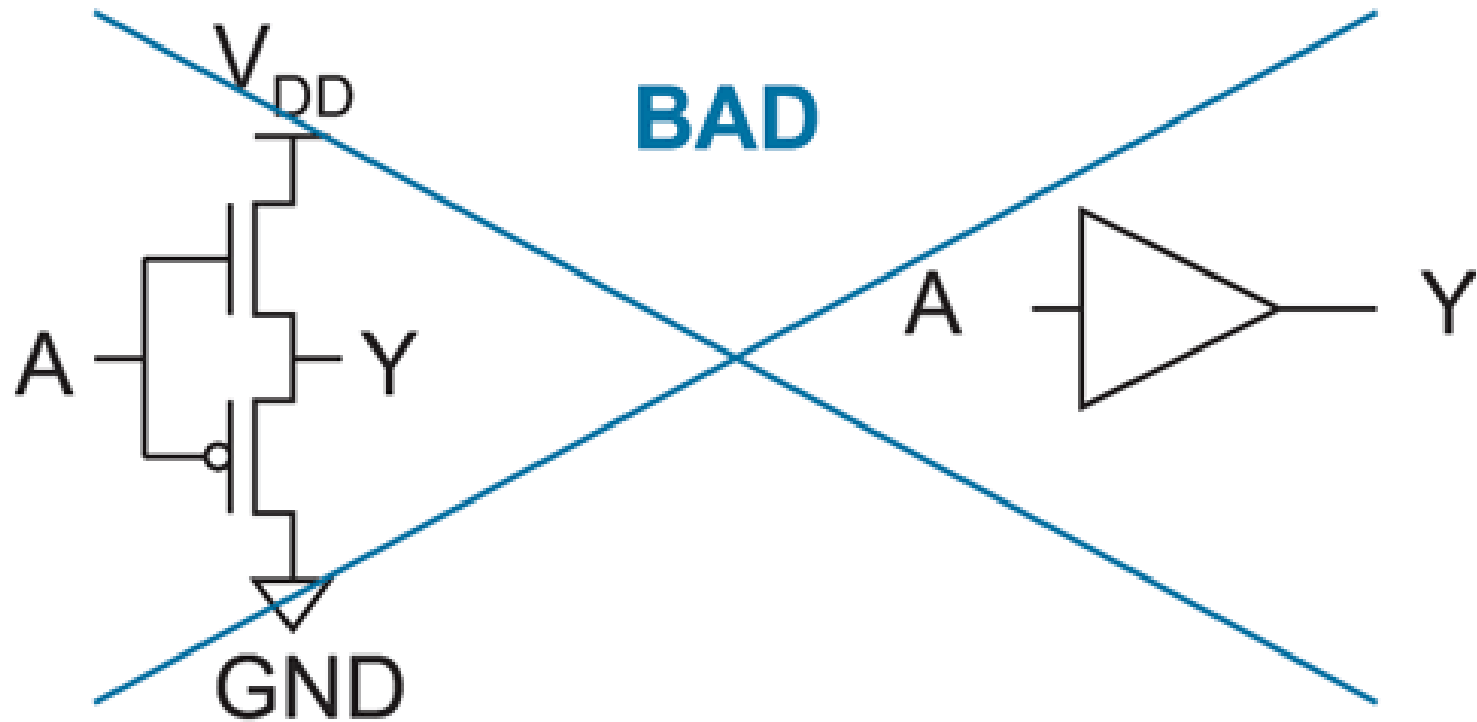- NMOS used for pull-down, PMOS for pull-up

 




**FIG 1.21** Bad noninverting buffer

# CMOS Inverter


*The most widely used gate....*



**FIG 2.23** A CMOS inverter
 
# *Inverter Operation*

- Inverter is simplest digital logic gate




| In | Out |
|----|-----|
| 0  | 1   |
| 1  | 0   |

- Many different circuit styles possible
  - Resistive-load
  - Pseudo-NMOS
  - CMOS
- Important characteristics
  - Speed (delay through the gate)
  - Power consumption
  - Robustness (tolerance to noise)
  - Area and process cost
 
# *Inverter model: VTC*


Voltage transfer curve (VTC): plot of output voltage  $V_{out}$  vs. input voltage  $V_{in}$



## Ideal digital inverter:


- When  $V_{in}=0$ ,  $V_{out}=V_{cc}$
- When  $V_{in}=V_{cc}$ ,  $V_{out}=0$
- Sharp transition region

# Actual inverter: $V_{OH}$ and $V_{OL}$

 

- $V_{OH}$  and  $V_{OL}$  represent the “high” and “low” output voltages of the inverter
- $V_{OH}$  = output voltage when  $V_{in} = '0'$
- $V_{OL}$  = output voltage when  $V_{in} = '1'$
- Ideally,
  - $V_{OH} = V_{CC}$
  - $V_{OL} = 0$

# *VOL and VOH*

 


□ In transfer function terms:

- $V_{OL} = f(V_{OH})$
- $V_{OH} = f(V_{OL})$
- $f$  = inverter transfer function

□ Difference ( $V_{OH} - V_{OL}$ ) is the *voltage swing* of the gate

- *Full-swing logic* swings from ground to  $V_{CC}$


# Inverter Threshold

 

Inverter switching threshold:

- Point where voltage transfer curve intersects line  $V_{out}=V_{in}$
- Represents the point at which the inverter switches state
- Normally,  $V_M \approx V_{CC}/2$


# CMOS Inverter Noise Margins

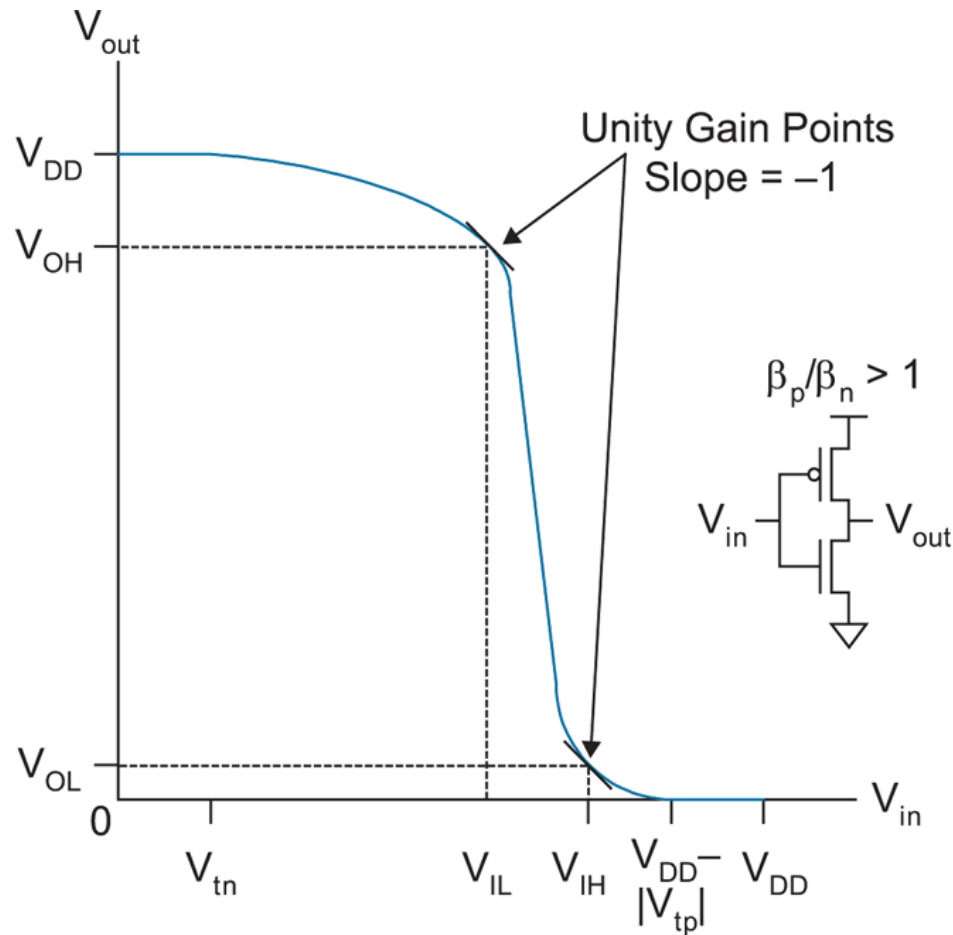

**FIG 2.28** CMOS inverter noise margins




# Noise Margins

 

- $V_{IL}$  and  $V_{IH}$  measure effect of input voltage on inverter output
- $V_{IL}$  = largest input voltage recognized as logic '0'
- $V_{IH}$  = smallest input voltage recognized as logic '1'
- Defined as point on VTC where slope = -1

# Noise Margin (cont)

 

Ideally, noise margin should be as large as possible

- Noise margin is a measure of the *robustness* of an inverter
  - $N_{ML} = V_{IL} - V_{OL}$
  - $N_{MH} = V_{OH} - V_{IH}$
- Models a chain of inverters. Example:
  - First inverter output is  $V_{OH}$
  - Second inverter recognizes input  $> V_{IH}$  as logic '1'
  - Difference  $V_{OH} - V_{IH}$  is "safety zone" for noise

# Noise Margin (cont)

□ Why are  $V_{IL}$ ,  $V_{IH}$  defined as unity-gain point on VTC curve?

- Assume there is noise on input voltage  $V_{in}$


$$V_{out} = f(V_{in} + V_{noise})$$

– First-order approximation (Taylor Series):

$$V_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} V_{noise}$$


- If gain ( $dV_{out}/dV_{in}$ )  $> 1$ , noise will be amplified.
- If gain  $< 1$ , noise is filtered. Therefore  $V_{IL}$ ,  $V_{IH}$  ensure that gain  $< 1$

# Noise Margin (summary)

 

**FIG 2.27** Noise margin definitions


# Inverter Time Response

 

□ Propagation delay measured from 50% point of  $V_{in}$  to 50% point of  $V_{out}$

□  $t_{pHL} = t_1 - t_0$ ,       $t_{pLH} = t_3 - t_2$ ,       $t_p = \frac{1}{2}(t_{pHL} + t_{pLH})$



# Rise and Fall Time

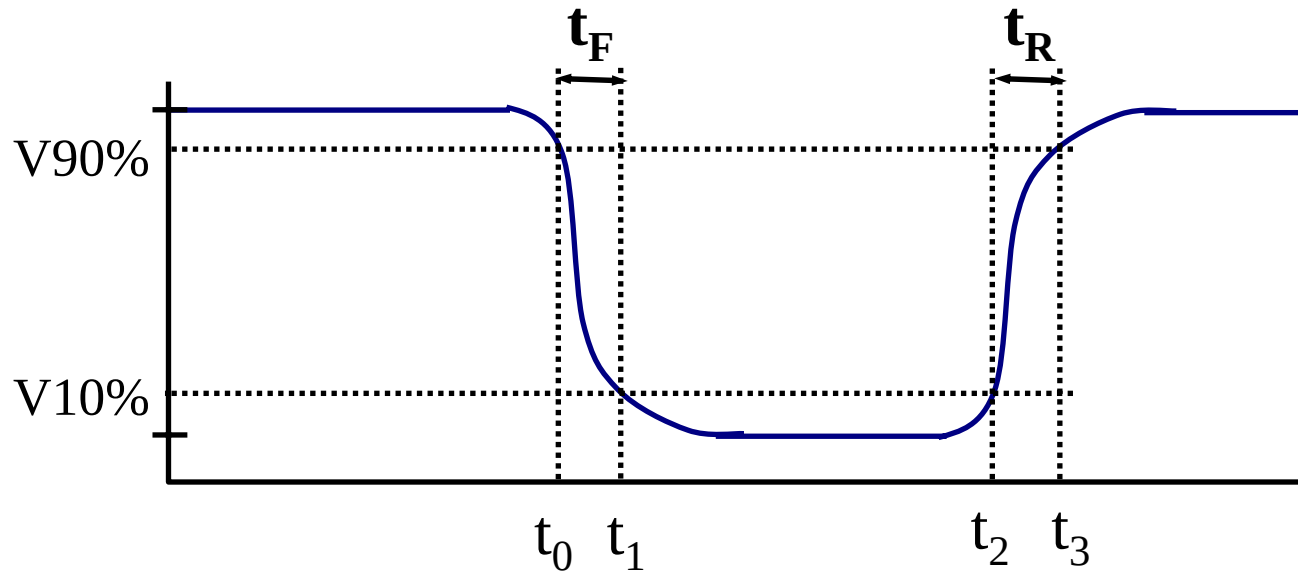

- ❑ Fall time: measured from 90% point to 10% point
  - $t_F = t_1 - t_0$
- ❑ Rise time: measured from 10% point to 90% point
  - $t_R = t_3 - t_2$
- ❑ Alternately, can define 20%-80% rise/fall time
  
# Ring Oscillator

- ❑ *Ring oscillator circuit*: standard method of comparing delay from one process to another
- ❑ Odd-number  $n$  of inverters connected in chain: oscillates with period  $T$  (usually  $n \gg 5$ )




$$T = t_{pLH1} + t_{pLH2} + t_{pLH3} + \dots$$

$$T = 2nt_p, \quad f = \frac{1}{T} = \frac{1}{2nt_p}, \quad t_p = \frac{1}{2nf}$$
 
# Resistive-load Inverter

- ❑ Requires only NMOS transistor and resistor
- ❑ When  $V_{in} = 0$ :
  - NMOS is OFF ( $V_{GS} = 0$ )
  - No current through NMOS or resistor
  - $V_{out} \approx V_{cc}$
- ❑ When  $V_{in} = V_{cc}$ :
  - NMOS is ON ( $V_{GS} = V_{cc}$ )
  - NMOS on resistance  $\ll R$
  - $V_{out} \approx 0$




*Not suitable for VLSI: large area of  $R$ , DC power dissipation.*



Remember: if body terminal not shown, it is connected to gnd for NMOS, vcc for PMOS




# Resistive-load Inverter

  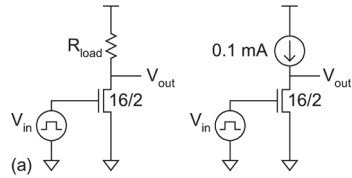

**FIG 2.29** Generic nMOS inverters with resistive or constant current load

 
# Pseudo-NMOS Inverter

- ❑ Replace resistor with “always-on” PMOS transistor
- ❑ Easier to implement in standard process than large resistance value
- ❑ PMOS load transistor:
  - On when  $V_{GS} < V_T \rightarrow V_{GS} = -V_{CC}$ : **transistor always on**
  - Linear when  $V_{DS} > V_{GS} - V_T \rightarrow V_{out} - V_{cc} > -V_{cc} - V_T \rightarrow V_{out} > -V_T$
  - Saturated when  $V_{DS} < V_{GS} - V_T \rightarrow V_{out} - V_{cc} < -V_{cc} - V_T \rightarrow V_{out} < -V_T$



Remember:  
 $V_T(\text{PMOS}) < 0$


# Pseudo-NMOS Inverter

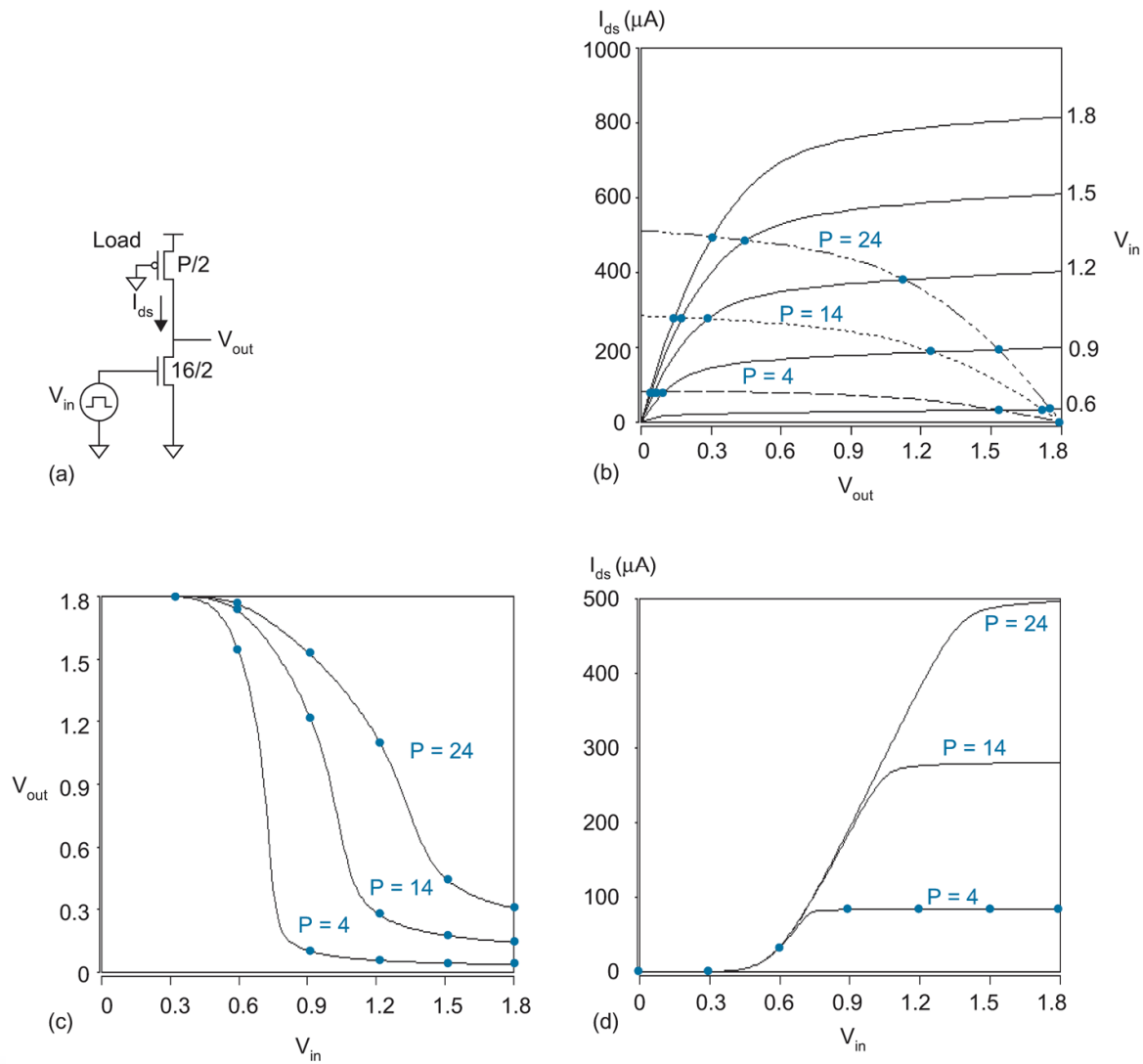



**FIG 2.30** Pseudo-nMOS inverter and DC transfer characteristics
 
# CMOS Inverter

- ❑ Complementary NMOS and PMOS devices
- ❑ In steady-state, only one device is on (no static power consumption)
- ❑  $V_{in}=1$ : NMOS on, PMOS off
  - $V_{out} = V_{OL} = 0$
- ❑  $V_{in}=0$ : PMOS on, NMOS off
  - $V_{out} = V_{OH} = V_{cc}$
- ❑ Ideal  $V_{OL}$  and  $V_{OH}$ !
- ❑ High input resistance (insulated gate) and low output impedance (finite resistance path between output and  $V_{cc}$  or Gnd)
- ❑ **Ratioless logic**





# CMOS Inverter

  

# Two Inverters



Share power and ground

Abut cells

  


# CMOS Inverter

## First-Order DC Analysis

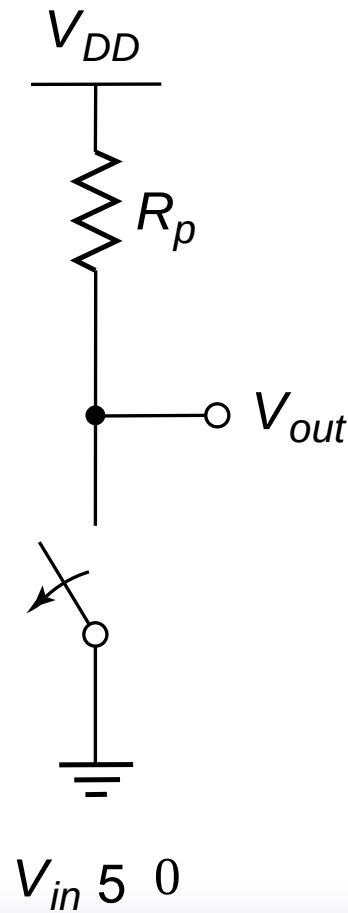 


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

# CMOS Inverter: Transient Response

 

(a) Low-to-high

 

(b) High-to-low

$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$



# CMOS Inverter Operation (summary)

| Table 2.2 Relationships between voltages for the three regions of operation of a CMOS inverter |                            |                              |                              |
|------------------------------------------------------------------------------------------------|----------------------------|------------------------------|------------------------------|
|                                                                                                | Cutoff                     | Linear                       | Saturated                    |
| nMOS                                                                                           | $V_{gsn} < V_{tn}$         | $V_{gsn} > V_{tn}$           | $V_{gsn} > V_{tn}$           |
|                                                                                                | $V_{in} < V_{tn}$          | $V_{in} > V_{tn}$            | $V_{in} > V_{tn}$            |
|                                                                                                |                            | $V_{dsn} < V_{gsn} - V_{tn}$ | $V_{dsn} > V_{gsn} - V_{tn}$ |
|                                                                                                |                            | $V_{out} < V_{in} - V_{tn}$  | $V_{out} > V_{in} - V_{tn}$  |
| pMOS                                                                                           | $V_{gsp} > V_{tp}$         | $V_{gsp} < V_{tp}$           | $V_{gsp} < V_{tp}$           |
|                                                                                                | $V_{in} > V_{tp} + V_{DD}$ | $V_{in} < V_{tp} + V_{DD}$   | $V_{in} < V_{tp} + V_{DD}$   |
|                                                                                                |                            | $V_{dsp} > V_{gsp} - V_{tp}$ | $V_{dsp} < V_{gsp} - V_{tp}$ |
|                                                                                                |                            | $V_{out} > V_{in} - V_{tp}$  | $V_{out} < V_{in} - V_{tp}$  |


# Generating the Inverter VTC

A. Translate PMOS I-V Relations into NMOS Variable Space using the following:

$$I_{Dsp} = -I_{Dsn}$$


$$V_{Gsn} = V_{in}; \quad V_{Gsp} = V_{in} - V_{DD}$$
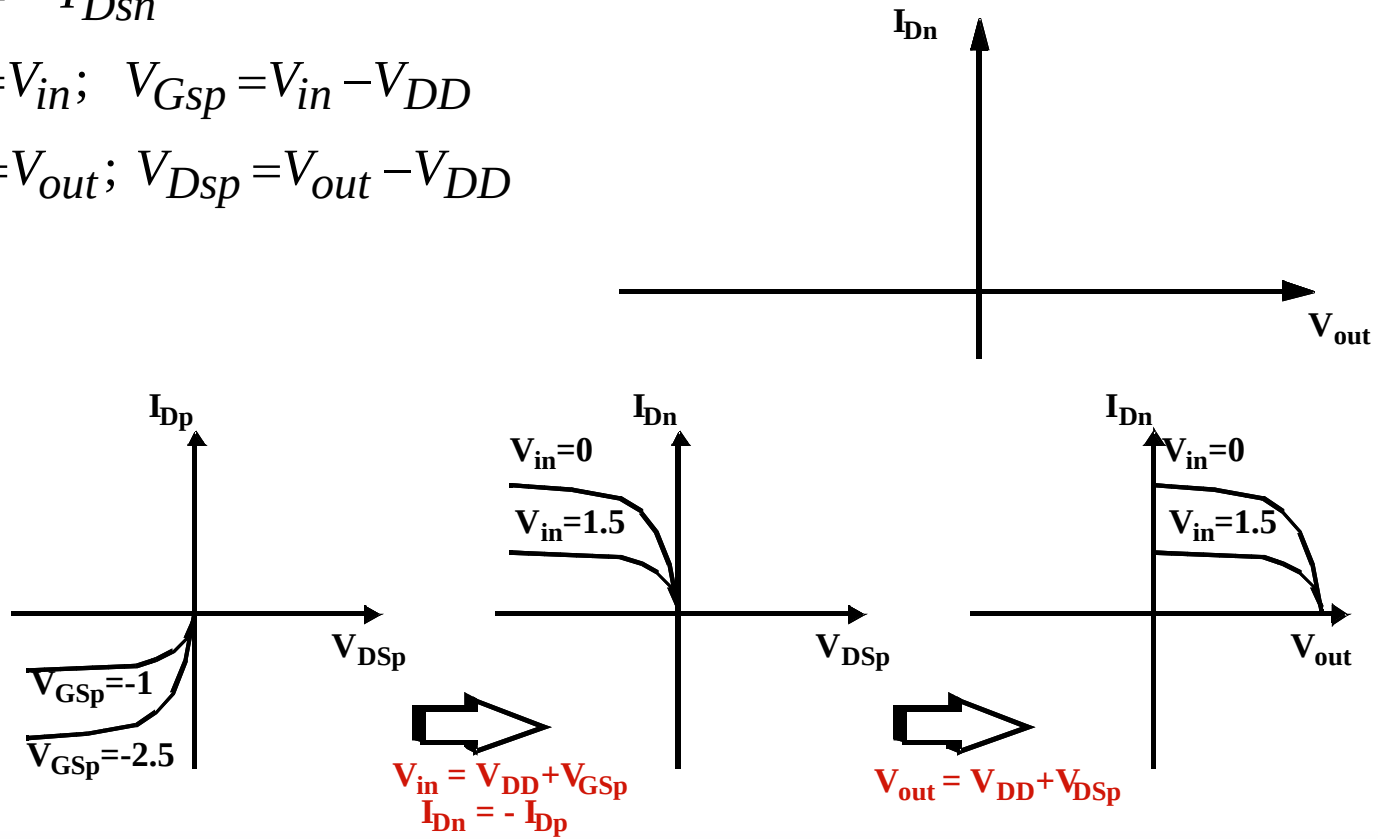
$$V_{Dsn} = V_{out}; \quad V_{Dsp} = V_{out} - V_{DD}$$




# CMOS Inverter Load Characteristics

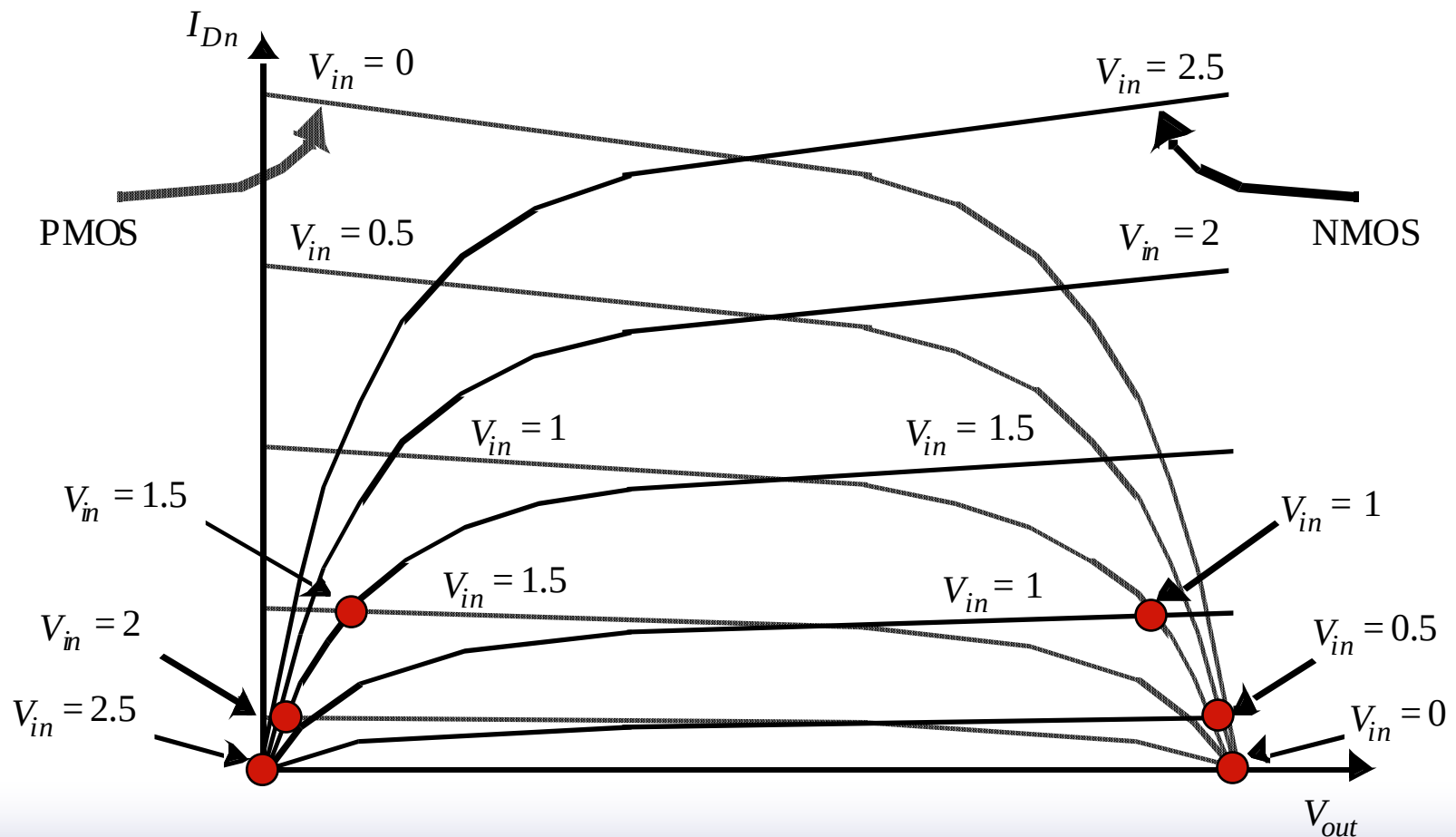*B. For a DC operating point to be valid, currents through NMOS and PMOS must be equal, hence find the points of intersection.*




# CMOS Inverter VTC

 


*In which state do the transistors spend most of their time?*
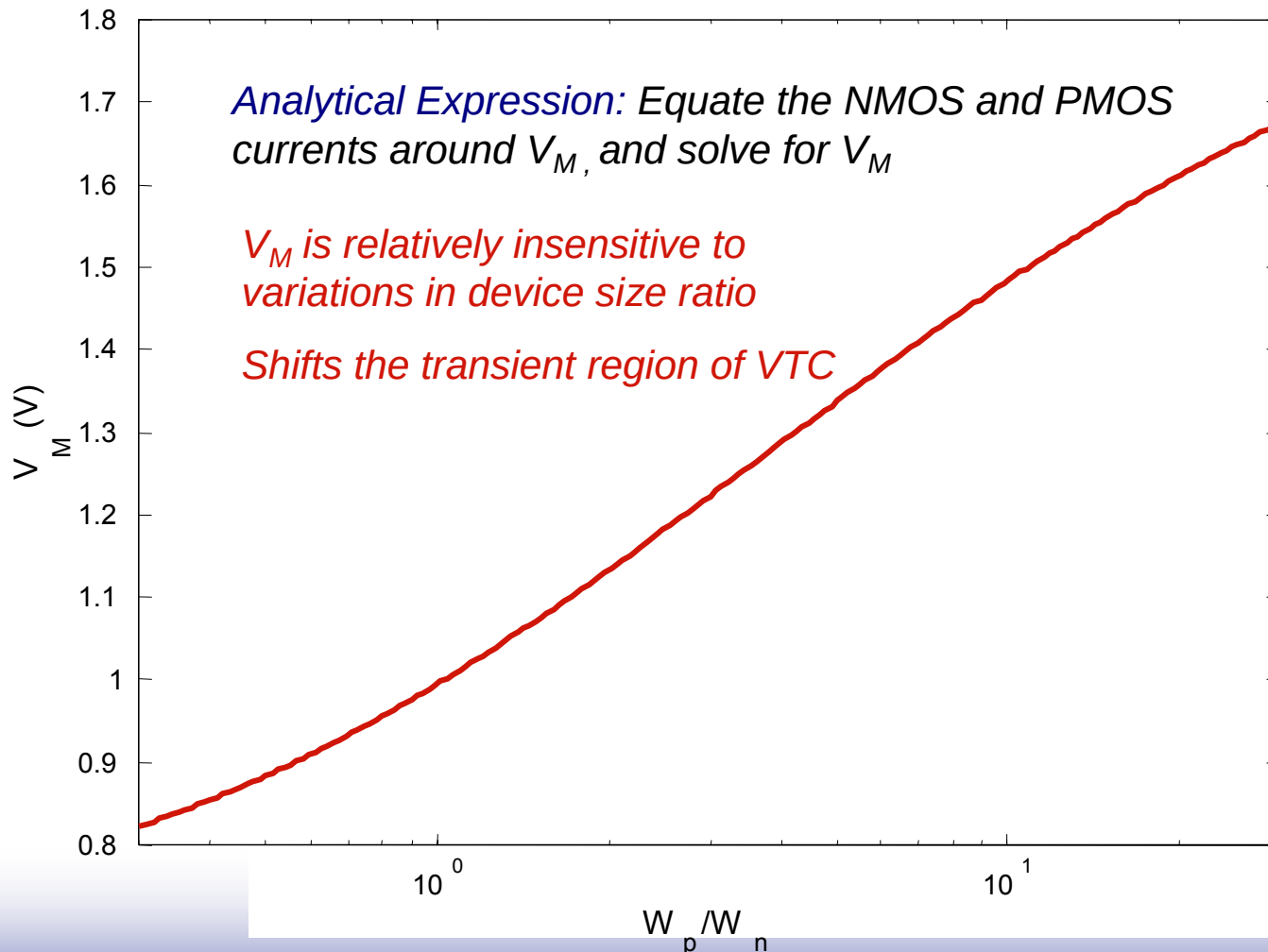
# Switching Threshold as a function of Transistor Ratio



# Determining $V_{IH}$ and $V_{IL}$

 

i.e.,  $V_{OH}=V_{DD}$  and  $V_{OL}=0$

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$


$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$

*Note: As  $g \rightarrow \infty$ ,  $V_{IH} = V_{IL} = V_M$ ,  
i.e., ideal inverter*


A simplified approach: piecewise linear approximation of the VTC

# Simulated VTC

 

Note: piecewise linear approximation of the VTC would lead to higher gain

# Inverter Gain

 


*Gain is mostly determined by technology parameters, especially channel length modulation, but also by  $V_{DD}$*

*Note: approximately  $V_M \propto V_{DD}$*




# Inverter Skew

 


**FIG 2.26** Transfer characteristics of skewed inverters

# The Transistor as a Switch

 

$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$

# *The Transistor as a Switch*

 


# The Transistor as a Switch

**Table 3.3** Equivalent resistance  $R_{eq}$  ( $W/L = 1$ ) of NMOS and PMOS transistors in 0.25  $\mu\text{m}$  CMOS process (with  $L = L_{min}$ ). For larger devices, divide  $R_{eq}$  by  $W/L$ .

| $V_{DD}$ (V)       | 1   | 1.5 | 2  | 2.5 |
|--------------------|-----|-----|----|-----|
| NMOS ( $k\Omega$ ) | 35  | 19  | 15 | 13  |
| PMOS ( $k\Omega$ ) | 115 | 55  | 38 | 31  |

# *Propagation Delay*

# CMOS inverter capacitances

 

## Cap on Node f:

- Junction cap:  $C_{db,p}$  and  $C_{db,n}$
- Gate (overlap) capacitance  $C_{gd,p}$  and  $C_{gd,n}$  (beware of Miller effect)
- Interconnect cap:  $C_{int}$
- Receiver gate cap:  $C_g$

# CMOS inverter capacitances

$$C_{load} = \underbrace{C_{db,n} + C_{db,p}} + \underbrace{C_{gd,n} + C_{gd,p}} + C_{int} + \underbrace{C_{gate}}$$

$$C_{db,n}, C_{db,p} = AK_{eq}C_{j0} + PK_{eqsw}C_{jsw}$$


$$C_{gd,n}, C_{gd,p} = 2WL_D C_{ox}$$

↑  
Miller effect

$$C_{gate} = WL_{drawn} C_{ox}$$

↑  
For each gate

 
# CMOS Inverter Propagation Delay Approach 1




$$t_{pHL} = \frac{C_L V_{swing}/2}{I_{av}}$$



 
# CMOS Inverter Propagation Delay Approach 2


 
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$




# CMOS Inverters

 
 
# Transient Response

Due to  $C_{gd}$  of transistors: can affect gate performance



Symmetric inverter has  $t_{pHL} = t_{pLH}$

$$t_p = 0.69 C_L (R_{eqn} + R_{eqp})/2$$

$$R_{eq} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{7}{9} \lambda V_{DD} \right)$$

with  $I_{DSAT} = k' \frac{W}{L} \left( (V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$


# *Design for Performance*

- ❑ Keep load capacitances ( $C_L$ ) small
  - Recall that three major components contribute to the load cap.
    - internal diffusion + overlap caps
    - interconnect cap.
    - fan-out (gate cap)
- ❑ Increase transistor sizes
  - watch out for self-loading!
- ❑ Increase  $V_{DD}$  (??)
  - watch out for reliability issues!

 
# Delay as a function of $V_{DD}$

Same as the ON resistance of a transistor....


Trade off energy dissipation vs performance.....



# Device Sizing

 


# NMOS/PMOS ratio

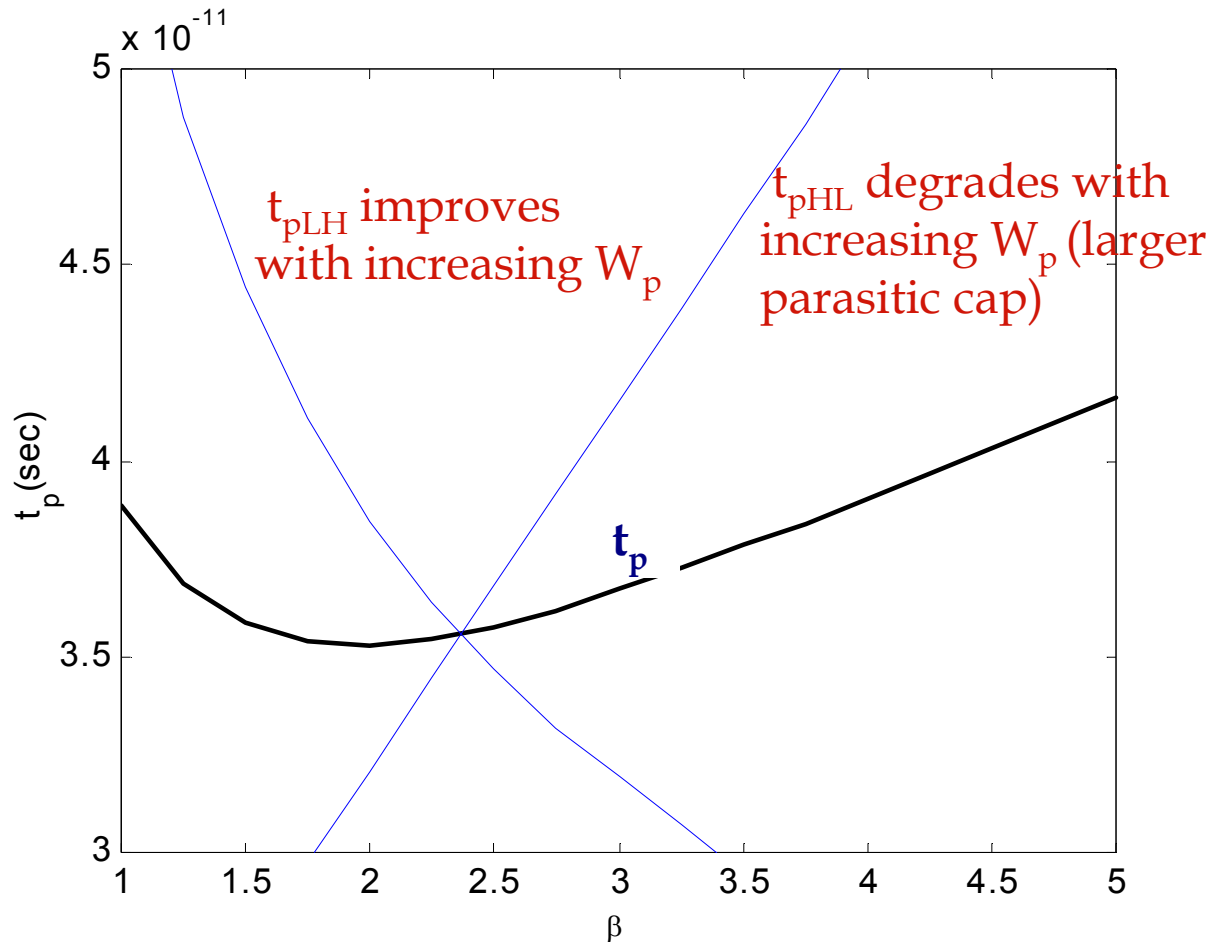

$$\beta = W_p/W_n$$

*If symmetry and noise margins are not of prime concern, inverter delay can be reduced by reducing the width of PMOS....*

# Impact of Rise Time on Delay

 

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$