
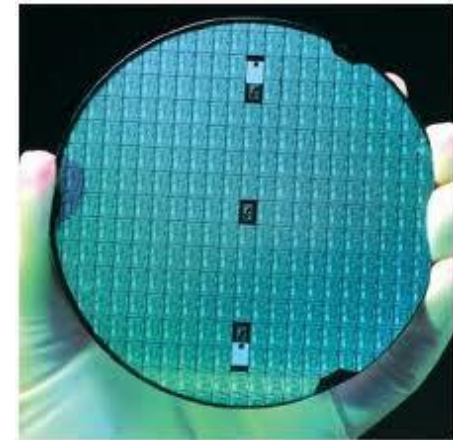
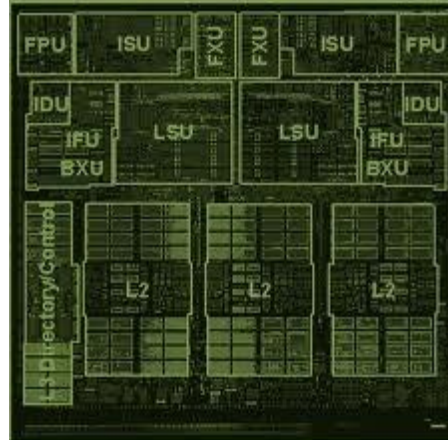


Structure of silicon crystal

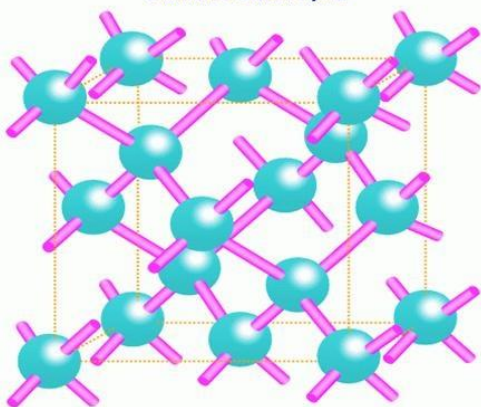

# ***ECE 225***

## ***Lecture 7***

### ***VLSI Interconnects-II***


*Prof. Kaustav Banerjee*  
*Electrical and Computer Engineering*  
*University of California, Santa Barbara*

# Outline

- Interconnect and Technology Scaling
  - Interconnect technology: background and trends
  - Interconnect Parasitics: R-L-C
  - Elmore Delay Formalism
  - ▪ Interconnect Scaling: implications for technology and design
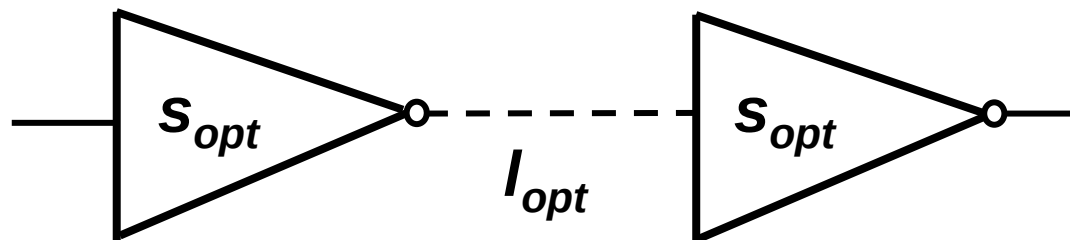
# Repeater Insertion


- Delay of wire increases quadratically with its length,  $L$  (delay =  $RC$ ...if unbuffered)
- **Repeater** (inverter) or **buffer** insertion results in lower delay increase....(delay =  $t_{inv} + RC/2$ ...if one inverter is inserted at  $L/2$ )
- Repeater size and inter-repeater separation can be optimized to give minimal delay



(from [Bakoglu89])
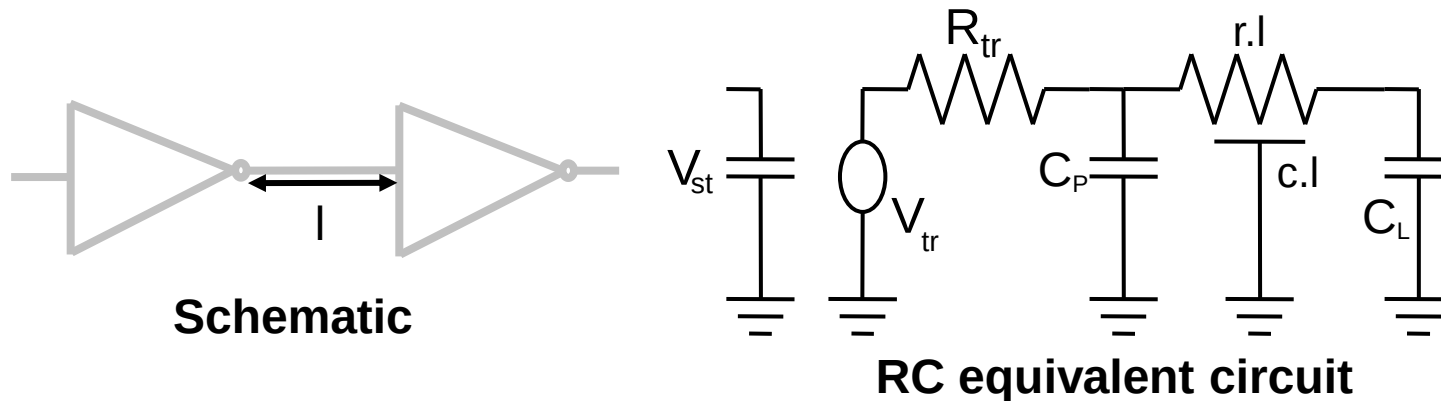
# Driver-Interconnect-Load Equivalent Circuit

- Interconnect segment of length  $l$  between two inverters



- $V_{st}$  is the voltage at the input capacitance that controls the voltage source  $V_{tr}$
- $R_{tr}$  is the driver transistor resistance,  $C_p$  is output parasitic capacitance
- $C_L$  is the load capacitance of next stage,  $r$  and  $c$  are interconnect resistance and capacitance per unit length respectively

# Interconnect Scaling

## Interconnect Scaling Scenarios

- ❑ Performance of a technology can be summarized by the time delay,  $t_d$ :

$$t_d = R_{tr} (C_P + C_L) + (R_{tr} c + r C_L) l + \frac{1}{2} r c l^2$$

intrinsic stage delay + load delay + interconnect delay

- ❑ If  $s$  is a scaling parameter: ratio of the feature size at a newer technology node to the feature size at an older node, then  $s < 1$
- ❑ Two simple scaling scenarios
  - ❑ scale metal pitch at constant thickness
  - ❑ scale metal pitch and the metal thickness

# *Interconnect Scaling*

## *Implications of Technology Scaling on Technology Performance*

- ❑ **Scaling metal pitch at constant thickness**
  - ❑ load delay, line delay, and current density will scale as  $1/s$ ,  $1/s^2$ , and  $1/s$  respectively.
- ❑ **Scaling metal pitch and the metal thickness**
  - ❑ load delay, line delay, and current density will scale as  $1/s^2$ ,  $1/s^2$ , and  $1/s^2$  respectively.
- ❑ **Hence, interconnect delay begin to dominate technology performance and current density increases with scaling**

# Interconnect Technology Scaling Trends

- ❑ Interconnect scaling requirements drive several technology enhancements:
  - ❑ use of low-dielectric constant **(low-k) materials** lowers the interconnect capacitance per unit length ( $c$ ) and therefore reduces the delay time
  - ❑ lower  $c$  helps in minimizing **cross-talk** noise
  - ❑ lower  $c$  also helps to reduce the **dynamic power** dissipation during switching of gates
  - ❑ lower interconnect resistance and higher current density requirements have driven the use of **new metallization**, such as Cu

# VLSI Interconnects

- ❑ Scaling of interconnects makes them slower, unlike scaling of devices
- ❑ **Local interconnects:** metal levels M1-M2, very densely packed (congested), follow transistor scaling, short distances (few  $\mu\text{m}$ )
- ❑ **Global interconnects:** top 3-4 metal levels (M7-M10) fewer such wires, more room for wide wires (not scaled aggressively), long distances (100s of  $\mu\text{m}$  or few mms)
- ❑ As devices switch faster, signal propagation delay on interconnects becomes appreciable fraction of intrinsic gate delay (at local/semi-global level) or much larger than gate delay (at global level)



# *Local Interconnects*

- ❑ Delay is small (but increasing) fraction of intrinsic gate delay
  - R-C models suffice
  - Capacitance more important than resistance
- ❑ Nanometer scale effects – scattering at surfaces and grain boundaries makes resistivity increase with scaling dimensions
- ❑ Small cross-section, high current density, electromigration reliability big problem
  - Fundamental limitation of material
  - Carbon nanomaterials can circumvent this limitation

# *Global Interconnects*


- ❑ Delay is a major challenge – limits speed of critical signal transmission like clock
- ❑ Simple R-C models inaccurate
- ❑ Beyond 100um lengths, few GHz frequencies, R becomes comparable to  $\omega L$
- ❑ Electromagnetic interactions beyond immediate neighbors become important
- ❑ Impedance (R, L) frequency dependent (skin and proximity effects): no formulae; field solvers or heuristic calculations

# *Global Interconnects*


- ❑ Thousands of large repeaters on-chip to control delay: power dissipation (clock network ~ 60-70% of total chip power)
- ❑ **Power-optimal repeater insertion** to save power on non-critical signal lines
- ❑ **3-D ICs**: short (~50um) vertical interconnects replace long (few mm) horizontal interconnects
- ❑ Carbon nanomaterials (CNTs, GNRs) based interconnects expected to have better performance and power dissipation than Cu
 
# Definition of Inductance ( $L$ )

$L_{ij}$  = geometrical constant of proportionality between the magnetic flux through victim loop  $j$  and the current running on aggressor loop  $i$  causing it


 
$$L_{ij} = \frac{\Psi_{i \rightarrow j}}{I_i} = \frac{1}{I_i} \int_{S_j} \mathbf{B}^{(i)} \cdot d\mathbf{S}_j$$



$$L_{ij} = \frac{\mu_0}{4\pi} \oint_{C_j} \oint_{C_i} \frac{d\boldsymbol{\ell}_j \cdot d\boldsymbol{\ell}_i}{|\mathbf{r}_j - \mathbf{r}_i|}$$

# On-Chip Inductance

- ❑ L starts to play a role at high GHz frequencies
- ❑ Effect increases for Cu: lower resistivity
- ❑ Can increase interconnect delay
- ❑ Can cause overshoot and undershoot effects
- ❑ Can cause switching noise:  $L di/dt$  voltage drops

$$Z = R + j\omega L$$

*inductance of a wire surrounded by a uniform dielectric:*

$$c \ell = \epsilon \mu$$

*c = cap. per unit length*

*l = inductance per unit length*

*From Maxwell's Laws:*

$$v = \frac{1}{\sqrt{\ell c}} = \frac{1}{\sqrt{\epsilon \mu}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$


*v = propagation speed of EM wave*

*c<sub>0</sub> = speed of light in vacuum = 30 cm/ns*

# *Accurate Interconnect Inductance Extraction*

- ❑ Requires full 3-D electromagnetic simulation
- ❑ FASTHENRY (from MIT) is a widely used tool in academia
  - See M. Kamon, M. J. Tsuk, and J. K. White, “FASTHENRY: A multipole-accelerated 3-D inductance extraction program,” IEEE Trans. Microwave Theory Techn., vol. 42, pp. 1750–1758, Sept. 1994.
  - Can be time consuming for complex interconnect topologies
  - Has limitations at very high frequencies

# Wire Length Dependency of L Effects

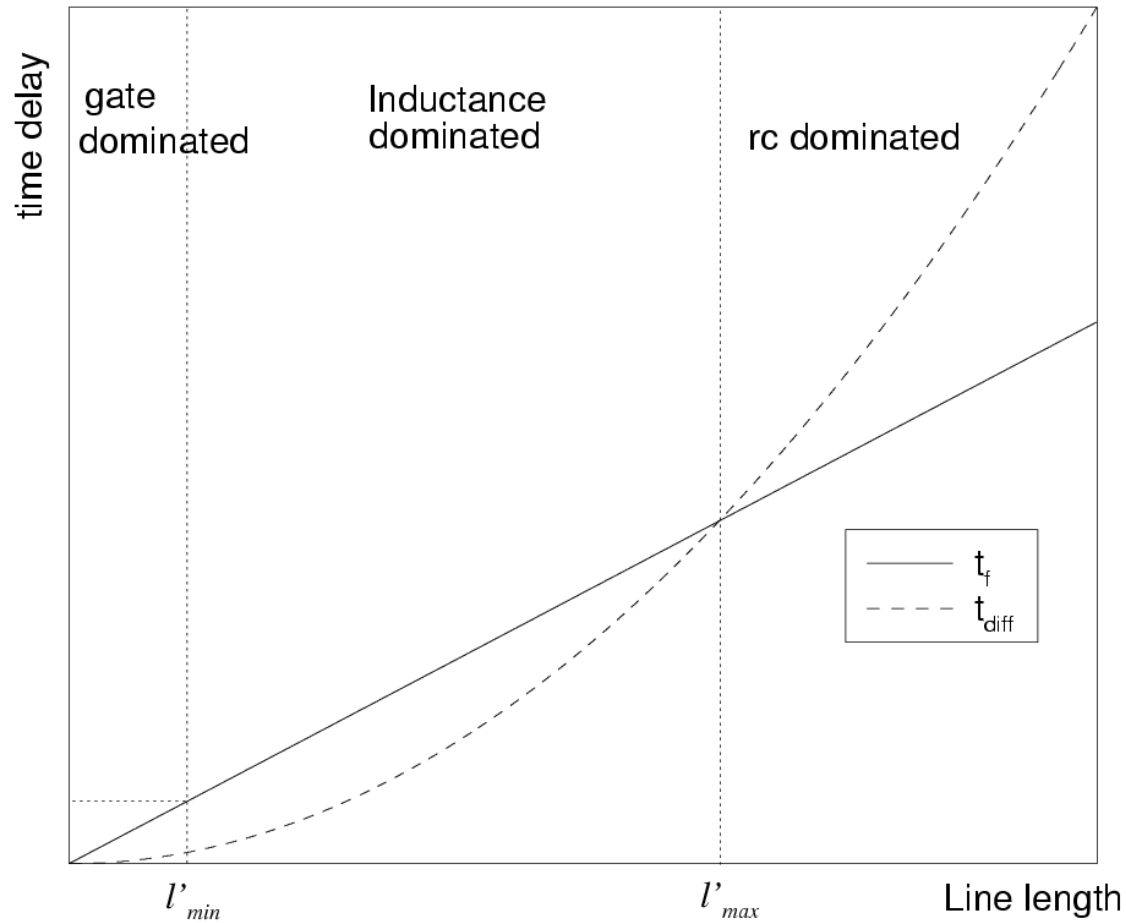

$$l'_{min} = \frac{T_{rise} v}{2}$$

$$l'_{max} = \frac{2Z_0}{r}$$

Suaya et al., Advanced Metallization Conf. 2006

# RLC Delay: Design Rules of Thumb

Wires in RLC domain:

$$t_{50\%} = \sqrt{LC} + \frac{\tau_{FO4}}{2} + 0.7Z_0C_{load} \quad \text{if}$$

$$\frac{rL}{Z_0} < 2\ln\left(\frac{4Z_0}{R_{driver} + Z_0}\right), \quad R_{driver} < 3Z_0$$

$$\text{where } Z_0 = \sqrt{l/c}$$

*Also see: A. Deutsch, et al., “When are transmission-line effects important for on-chip interconnections?,” IEEE Trans. Microwave Theory Tech., vol. 45, pp. 1836–1846, Oct. 1997.*




# *On-Chip Inductance Effects*

***K. Banerjee and A. Mehrotra, IEEE Transactions on Computer-Aided Design of Integrated Circuits and Systems, Vol. 21, No. 8, pp. 904-915, August 2002.***


# *On-Chip Inductance Effects*

- *Increasing clock speeds and decreasing rise times cause inductive effects*
- *Low resistance wires more susceptible to inductive effects*
  - *Global wires that are usually wide*
  - *introduction of Cu: lower resistivity*
- *Line inductance depends on current return path*
  - *strongly dependent on circuit topology*
  - *difficult to extract accurately*
  - *large variations*

# Step Response of an RLC Line

 

# Time-Domain Response of RLC Segment

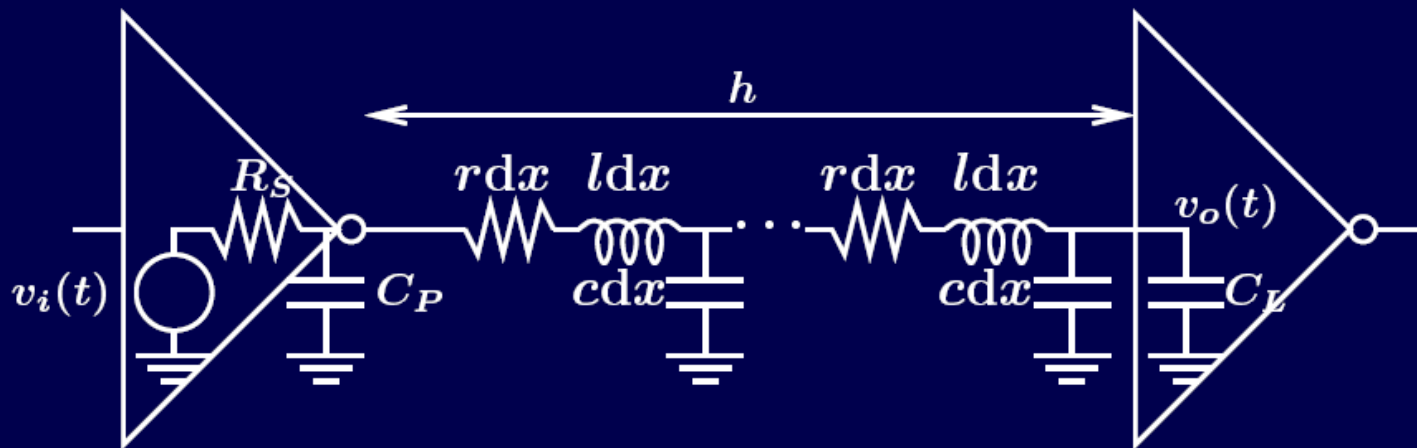

$$H(s) = \frac{1}{[1 + sR_S(C_P + C_L)] \cosh(\theta) + \left[ \frac{R_S}{Z_0} + sC_L Z_0 + s^2 R_S C_P C_L Z_0 \right] \sinh(\theta)}$$

$$\approx \frac{1}{1 + sb_1 + s^2 b_2 + s^3 b_3 + s^4 b_4}$$

$$Z_0 = \sqrt{\frac{r + sl}{sc}} \quad \theta = \sqrt{(r + sl)sc}h$$

# Critical Inductance


- Second order Padé expansion of  $H(s)$

$$H(s) \approx \frac{1}{1 + b_1 s + b_2 s^2}$$

- System overdamped, critically damped or underdamped when  $b_1^2 - 4b_2$  is  $>, =, < 0$ .
- At optimum buffer size and interconnect length, find  $l_{crit}$  for which the system is critically damped.
- For  $l <, =, > l_{crit}$ , the system is overdamped, critically damped or underdamped

# Impact of Scaling: Case 1


## Minimum Width Global Wires

 

- As technology scales,  $I < I_{crit}$  over larger range of line inductance
- Hence, impact of inductance **reduces** with scaling

# Impact of scaling: Case 2

## Unscaled Global Wires

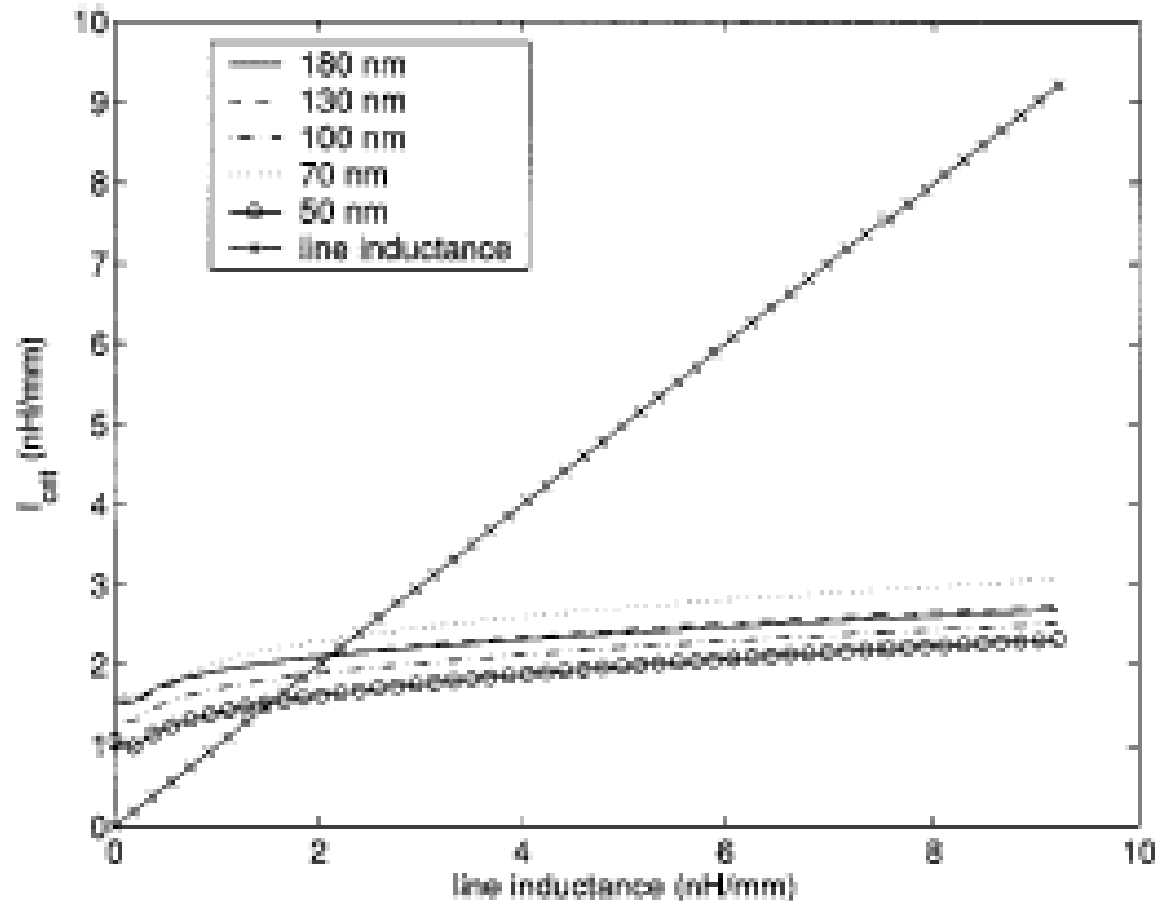

- As technology scales,  $I > I_{crit}$  over larger range of line inductance
- Hence, impact of inductance **increases** with scaling

# *High-Frequency Issues*



*K. Banerjee, S. Im and N. Srivastava, Proc. Advanced Metallization Conf., 2005.  
S. Suaya, R. Escovar, S. Ortiz, K. Banerjee and N. Srivastava, Proc. Advanced  
Metallization Conf., 2006.*



# *High-Frequency Effects*

- Frequency of signals on interconnects is rising rapidly
- Frequency dependent impedance extraction is a major hurdle
  - Field solvers are unable to handle the complexity of VLSI interconnects
- Need to develop models for interconnect geometry dependent calculation of high frequency impedance

# Signal Frequency on Interconnects

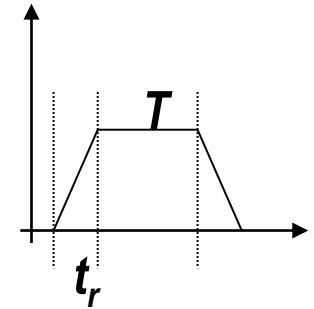 


Digital signal composed of various frequency components.

**Significant Frequency:**

Frequency used for interconnect analysis
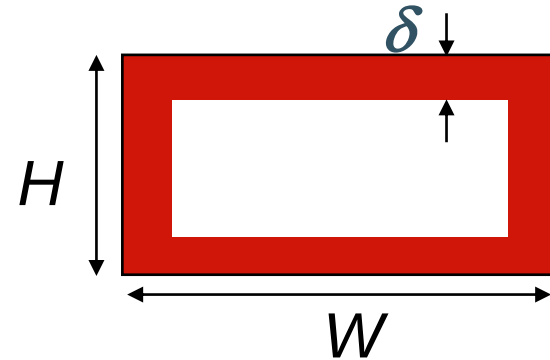
# Frequency Dependence of $R$

- At high enough frequencies,  $R$  can increase due to **skin effect**
- Current flow constrained in a thin layer along the surface of the conductor:  **$R$  increases**
- The current falls off exponentially with depth into the interconnect
- **Skin depth**,  $\delta$  is defined as the depth at which current falls off to a value of  $1/e$  of its nominal value



$$\delta = \sqrt{\frac{\rho}{\pi f \mu}}$$

$\mu$  is the permeability of the surrounding dielectric

Resistance per unit length:

$$r(f) = \frac{\sqrt{\pi f \mu \rho}}{2(H+W)}, \quad \text{for } W, H \gg \delta$$

# Skin Effect


- Onset of skin effect:  
at  $f=f_s$ ,  $\delta = 1/2 \times$   
smallest dimension

$$f_s = \frac{4\rho}{\pi\mu(\min(W,H))^2}$$

- For Cu wires:


| Freq                   | 1 GHZ | 5 GHZ | 10 GHZ | 15 GHZ | 20 GHZ |
|------------------------|-------|-------|--------|--------|--------|
| Skin depth ( $\mu m$ ) | 2.08  | 0.93  | 0.66   | 0.53   | 0.46   |

# Skin and Proximity Effects

 


*Isolated Wire  $5\mu\text{m} \times 5\mu\text{m}$*

 ***Skin Effect in  
Isolated  
Conductors***




*Isolated Wire  $5\mu\text{m} \times 1\mu\text{m}$*

 ***Proximity  
Effect in  
Coupled  
Conductors***



# Frequency Dependence of R and L

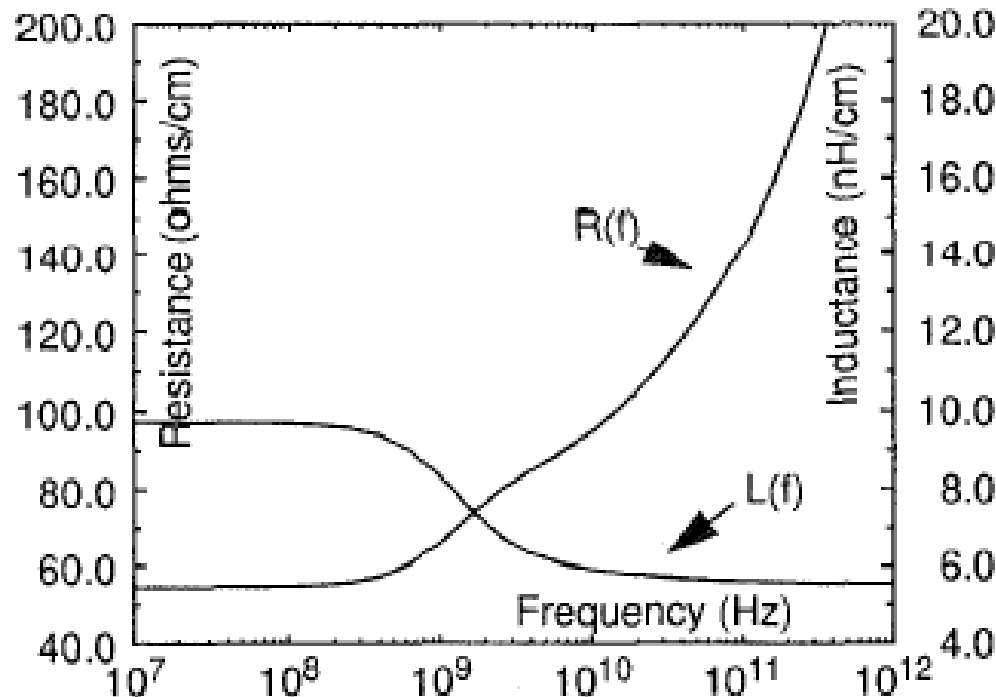


*B. Krauter and S. Mehrotra, DAC, 1998.*

- Resistance increases due to skin effect
- For lower frequencies, current return path is distributed between all ground lines---thus **loop inductance** is higher and return path resistance is smaller.....
- For higher frequencies, current returns through closest ground paths---thus loop area is smaller, hence loop inductance reduces and return path resistance increases
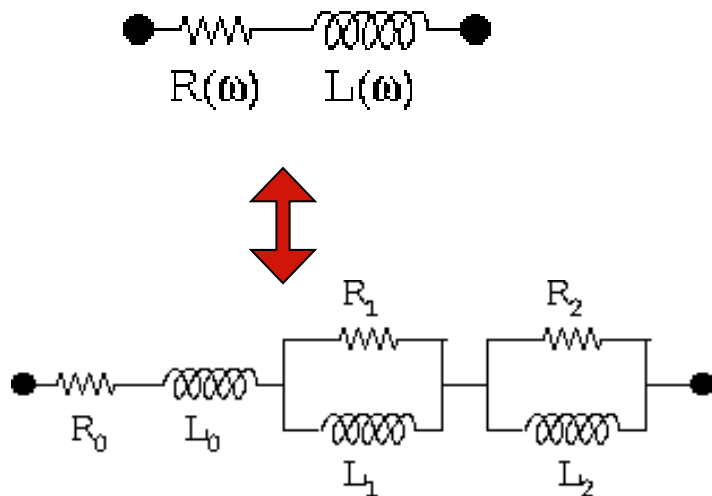
# Modeling Frequency Dependent Behavior


Replacing  $R(\omega), L(\omega)$  with Foster Pairs



Note that at smaller frequencies  $L_1$  ( $Z=j\omega L$ ) will short  $R_1$


$R_0$  and  $L_0+L_1+L_2$  are low-frequency values of  $R$  and  $L$

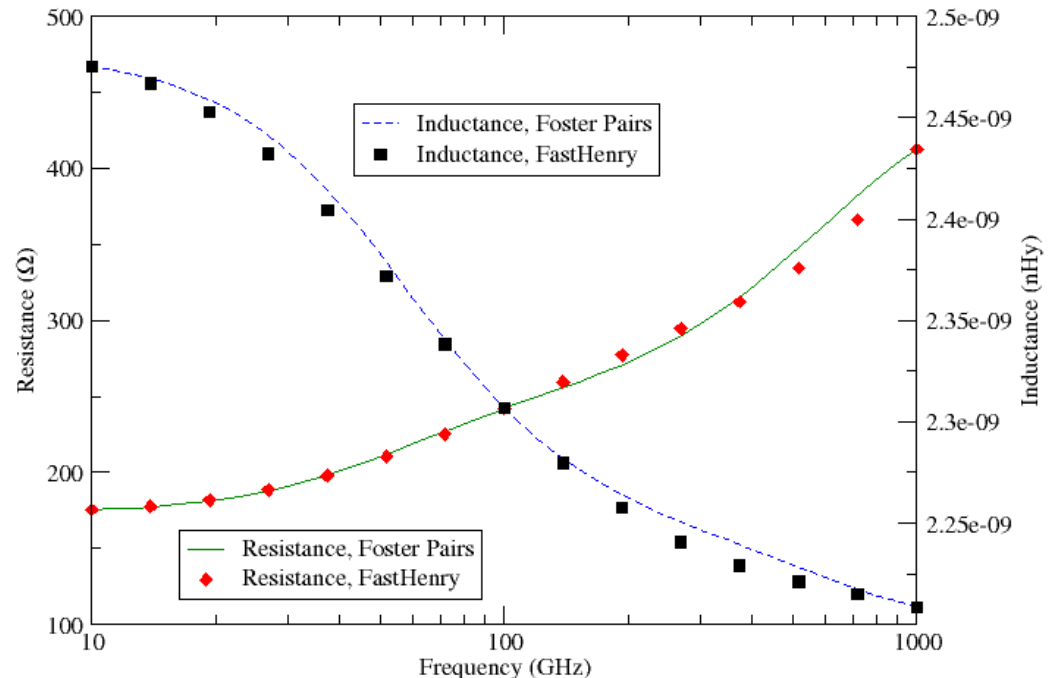At higher frequencies some current flows through  $R_1$  and  $R_2$ , hence  $R$  increases with frequency and effective inductance decreases



Suaya et al., Advanced Metallization Conf. 2006

# Substrate Effects

 

See, *N. Srivastava, R. Suaya and K. Banerjee, IEEE TCAD, Vol. 28, No. 7, pp. 1047-1060, July 2009.* ----Interconnect/inductor impedance extraction methodology in presence of multilayered conducting substrates – a **core technology in CALIBRE xL, xACT, tools by Mentor Graphics.**